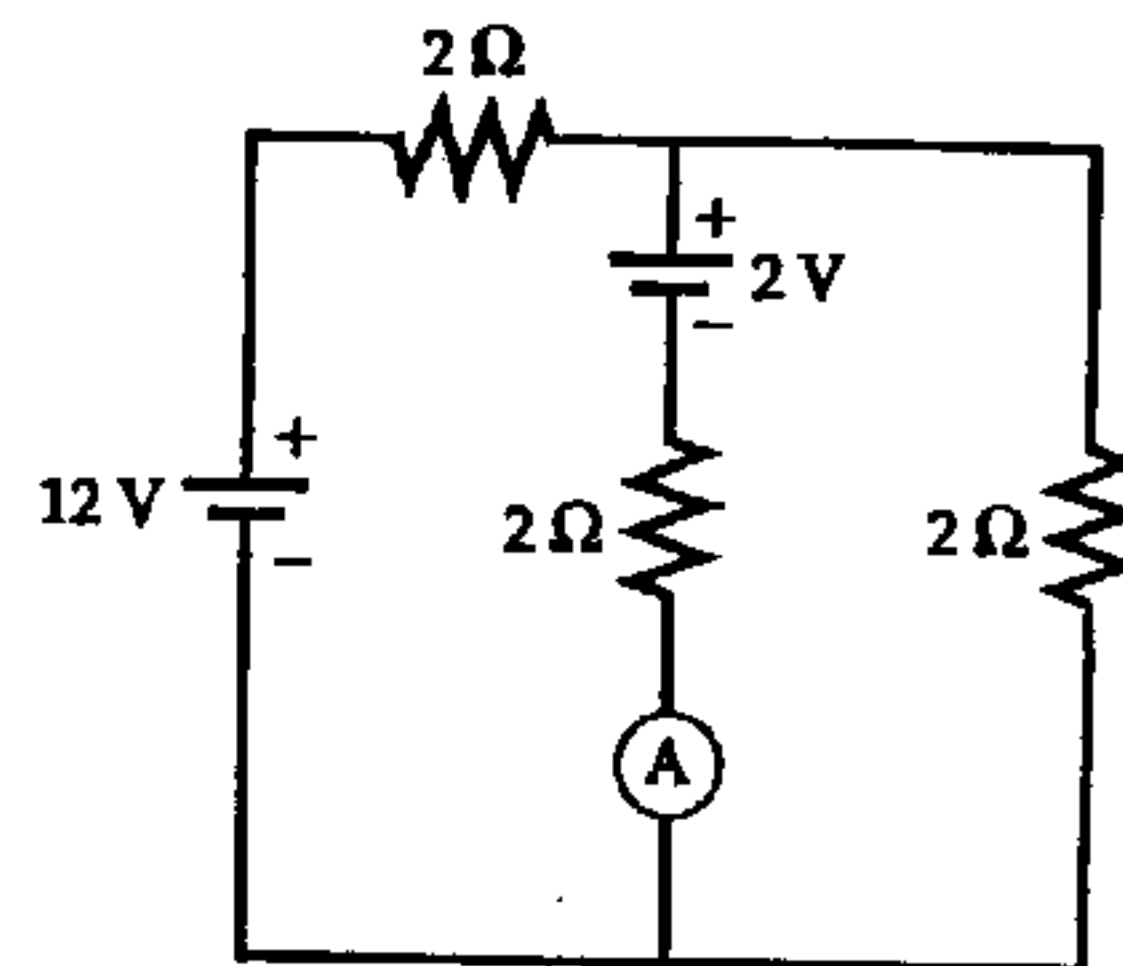


12 I. For the circuit to the right, determine the following. (The ammeter has negligible resistance.)

- 4 (a) The current through each resistor. Be sure to indicate direction as well as magnitude for each current.
- 2 (b) The power supplied by the 12V battery.
- 3 (c) The power dissipated in each resistor.
- 3 (d) Explain the difference in your answers to (b) and (c).





18 II. For the circuit shown below, determine

- 2 (a) The battery current immediately after the switch  $S$  is closed.
- 2 (b) The battery current a long time after  $S$  is closed.
- 2 (c) The potential difference across the  $600\text{k}\Omega$  resistor a long time after the switch is closed.
- 2 (d) The charge on the capacitor a long time after the switch is closed.

After the switch has been closed for a long time, it is opened. For this situation,

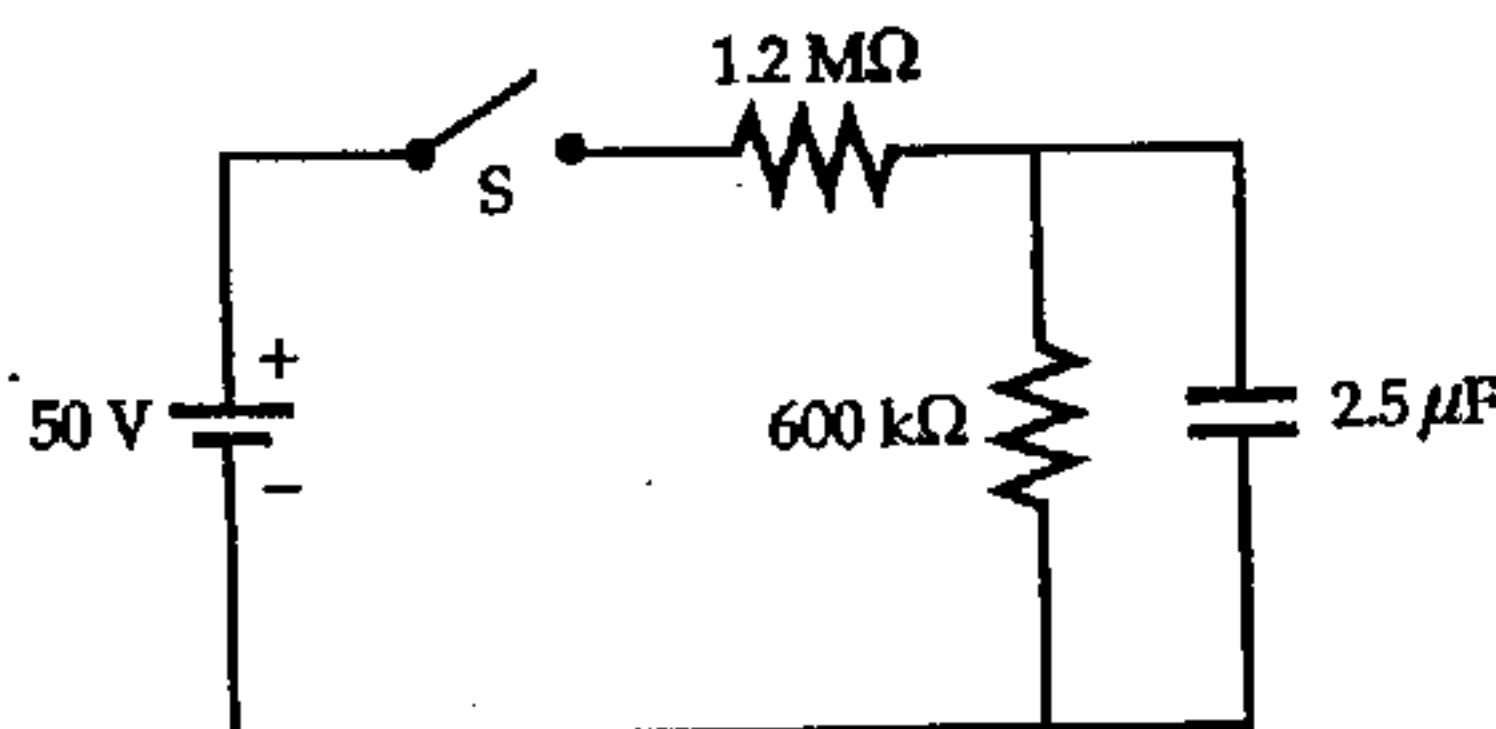- 5 (e) Determine  $I(t)$ , the current through the  $600\text{k}\Omega$  resistor, as a function of time.
- 2 (f) Sketch  $I(t)$ , indicating the value at  $t = 0$ .
- 3 (g) At what time after the switch is opened has the current fallen to 0.25 of its initial value?



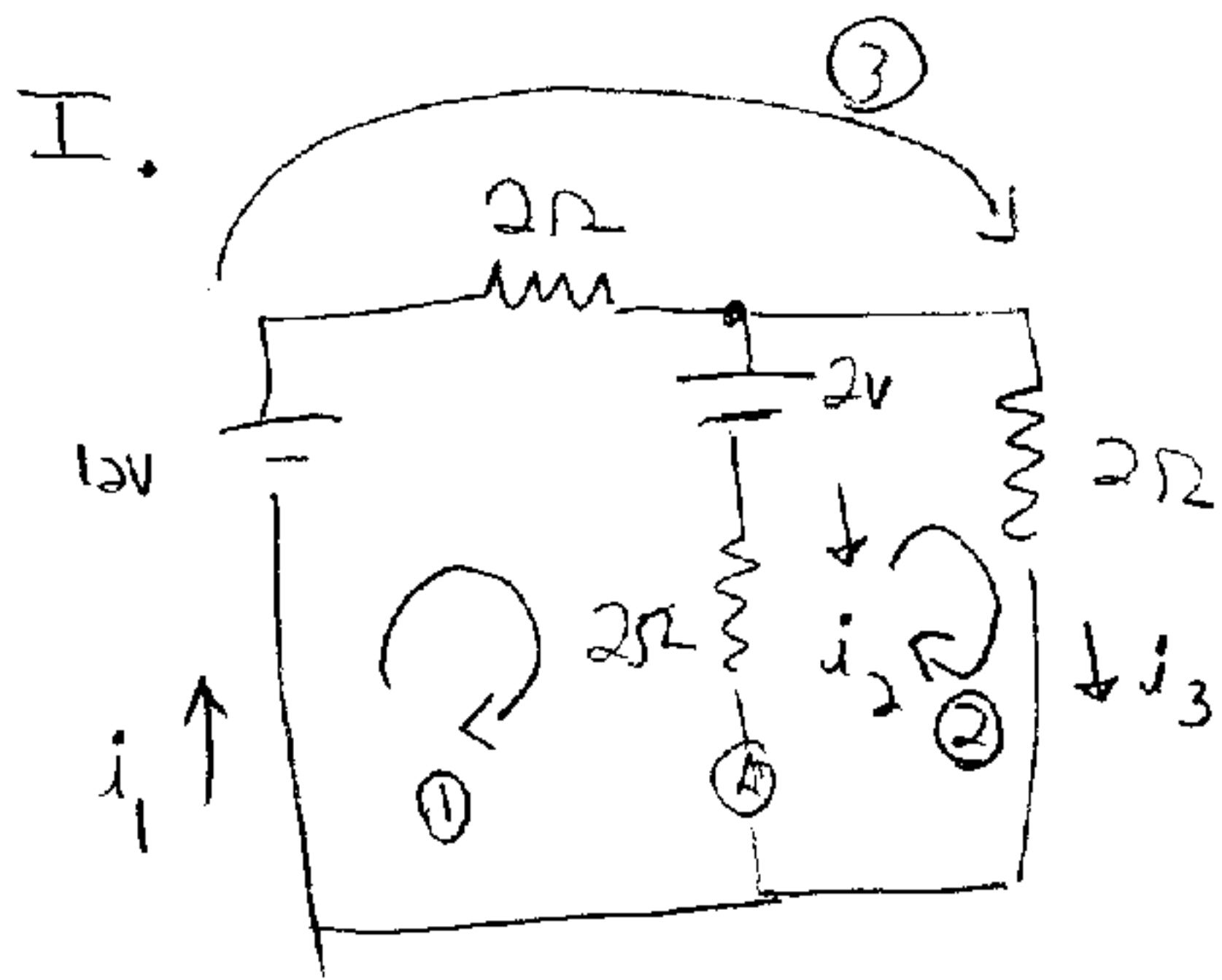

Need to set up Kirchhoff's law eqns:

$$i_1 = i_2 + i_3$$

$$\text{Loop ①: } 12 - 2i_1 - 2 - 2i_2 = 0$$

(Note that we traverse the 2V battery in the direction that the voltage drops!)

$$\text{Loop ②: } -2i_3 + 2i_2 + 2 = 0$$

$$\text{Loop ③: } 12 - 2i_1 - 2i_3 = 0$$

(a)

$$\text{Loop 1: } 5 = i_1 + i_2$$

$$+ 6 = 2i_1 - i_2$$

$$\parallel = 3i_1$$

$$i_1 = \frac{11}{3} \text{ A}$$

(up in figure)

$$\text{Loop 3: } 6 = i_1 + i_3 = i_1 + i_1 - i_2 = 2i_1 - i_2$$

$$i_2 = 5 - i_1 = \frac{15}{3} - \frac{11}{3} = \frac{4}{3}$$

$$i_2 = \frac{4}{3} \text{ A}$$

(down in figure)

$$i_3 = i_1 - i_2 = \frac{11}{3} - \frac{4}{3} = \frac{7}{3}$$

$$i_3 = \frac{7}{3} \text{ A}$$

(down in figure)

Check with Loop 2:

$$1 = i_3 - i_2 = \frac{7}{3} - \frac{4}{3} = \frac{3}{3} \checkmark$$

All currents are positive, so they are in the direction shown.

$$(b) \quad \mathcal{E} = IV = i_1 (12V)$$

$$\mathcal{E} = \left(\frac{4}{3} \text{ amps}\right) (12V)$$

$$\mathcal{E} = 44 \text{ watts}$$

$$(c) \quad P_1 = i_1^2 R_1 = \left(\frac{4}{3}\right)^2 \cdot 2$$

$$P_1 = \frac{121}{9} \cdot 2 = \frac{242}{9}$$

$$P_1 = 26.89W$$

$$P_2 = i_2^2 R_2 = \left(\frac{4}{3}\right)^2 \cdot 2$$

$$P_2 = \frac{32}{9}$$

$$P_2 = 3.56W$$

$$P_3 = i_3^2 R = \left(\frac{7}{3}\right)^2 \cdot 2$$

$$P_3 = \frac{98}{9}$$

$$P_3 = 10.89W$$

Total power dissipated in the resistors =  $41.33W = P_{TOT}$ ,  
which is  $< 44$  Watts


(d) The 12V battery delivers more power than is dissipated in the resistors. The additional energy is charging the 2V battery!  
Since  $i_2$  passes through the 2V battery from + to -, energy is delivered to the battery.

Check: Power delivered to 2V battery

$$\mathcal{E}_{2V} = i_2 V = \frac{4}{3} A (2V) = \frac{8}{3} \text{ watt} = 2.67W,$$

giving a total of 44W.

II.

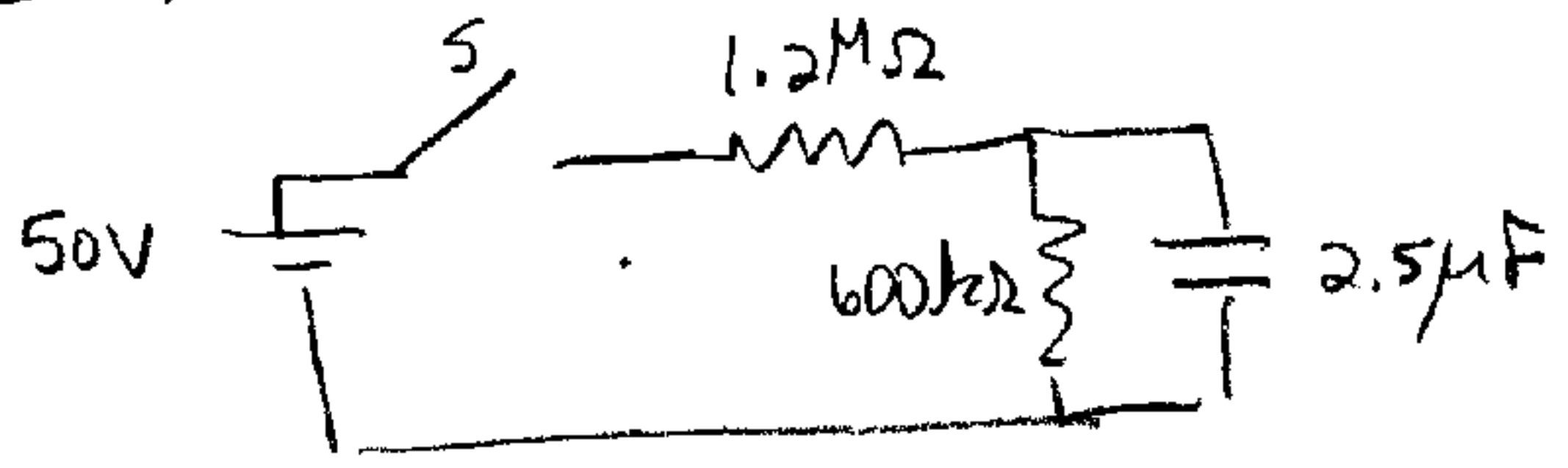

(a) Immediately after S is closed, the capacitor acts like a short & the 600 kΩ resistor is bypassed

$$I = \frac{50V}{1.2 \times 10^6 \Omega} = 41.7 \times 10^{-6} A$$

$$I(t=0) = 41.7 \mu A$$

(b) After the capacitor is charged, it acts like an open circuit

$$I = \frac{50V}{(1.2 + 0.6) \times 10^6 \Omega} = 27.8 \mu A$$

$$I(t=\infty) = 27.8 \mu A$$

$$(c) \Delta V_{600k\Omega} = IR = (27.8 \times 10^{-6} A)(.6 \times 10^6 \Omega) = 16.7 V$$

$$\Delta V_{600k\Omega} = 16.67 V$$

(d) The voltage drop across the 600 kΩ resistor = voltage drop across the capacitor

$$C = \frac{Q}{V} \quad \text{or} \quad Q = CV = (2.5 \times 10^{-6} F)(16.67 V)$$

$$Q = 41.67 \mu C$$

(d) Redefine  $t=0$  to be the time when the switch is opened.

When  $S$  is opened, the battery and the  $1.2\text{M}\Omega$  resistor are removed from the circuit. The capacitor discharges through the  $600\text{k}\Omega$  resistor.

$$I(t) = I_0 e^{-t/\tau}$$


$$\tau = RC = (0.6 \times 10^6 \Omega)(2.5 \times 10^{-6} \text{F}) = 1.5 \text{s}$$

$$\tau = 1.5 \text{s}$$

$$I_0 = \frac{V}{R} = \frac{16.7 \text{V}}{0.6 \times 10^6 \Omega} = 27.8 \mu\text{A}$$

$$I_0 = 27.8 \mu\text{A}$$

$$I(t) = 27.8 \mu\text{A} e^{-t/1.5}$$

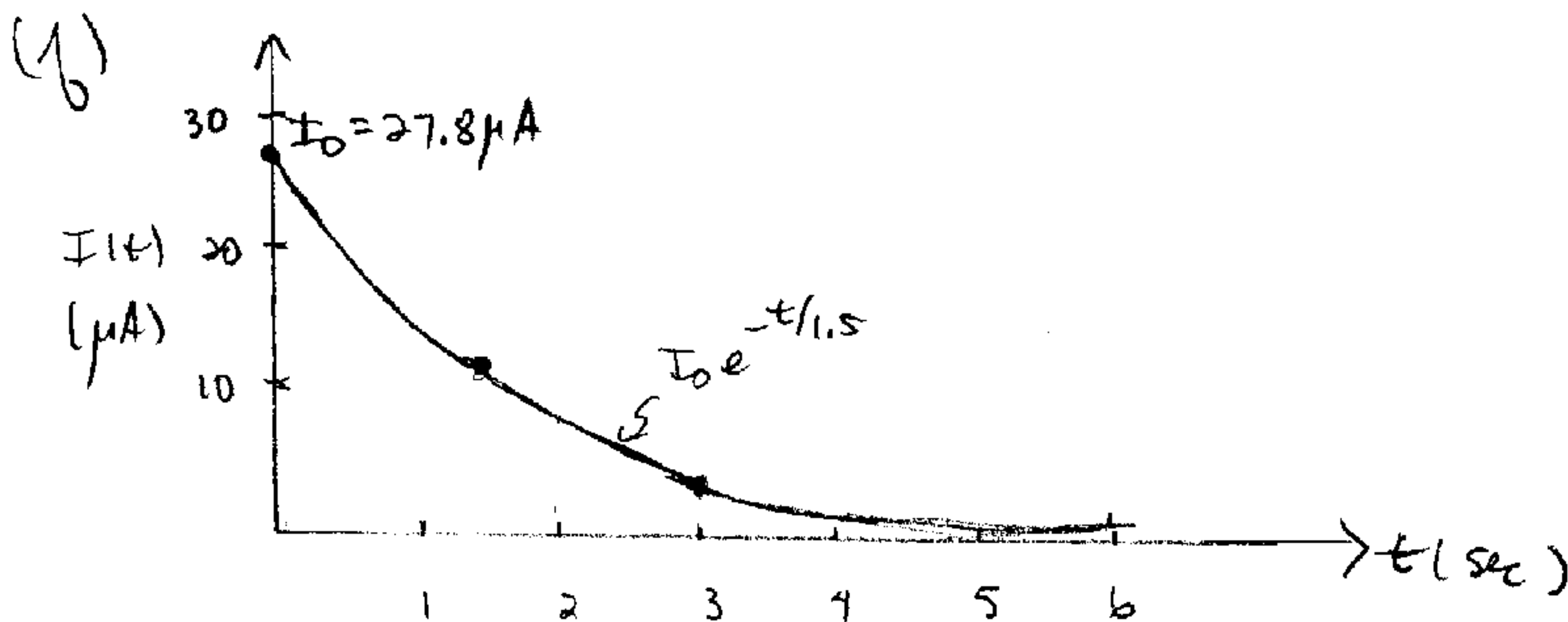

(g)  $I = I_0 e^{-t/\tau}$

$$\frac{I}{I_0} = 0.25 = e^{-t/\tau}$$

$$\ln(0.25) = -t/\tau$$

$$-\ln(0.25) \cdot \tau = t = 2.08 \text{s}$$

$$t_{0.25} = 2.08 \text{s}$$